

# Computer Architecture ECE314

## Winter 2004 Test 1

1. The fundamental gates are NOT, AND, OR, XOR. Draw and label the corresponding logic symbols and Verilog operators? (8 points)
  
  
  
  
  
  
  
  
  
  
2. Identify the following terms or abbreviations (2 points each)
  - (a) ASCII
  - (b) BCD
  - (c) MSB
  
3. Convert  $116_{10}$  to octal, hexadecimal and binary. (6 points)
  
  
  
  
  
  
  
  
  
  
4. Convert the binary number 00101011 to an 8-bit 2's-complement negative number. (3 points)
  
  
  
  
  
  
  
  
  
  
5. What are the differences between a flip-flop and a latch? (2 points)
  
  
  
  
  
  
  
  
  
  
6. Explain the hierarchical nature of a computer system. (5 points)
  
  
  
  
  
  
  
  
  
  
7. What common computer operation or principle is expressed by a 2:1 multiplexor? (2 points)

8. Define or explain the following terms (3 points each)


(a) tri-state buffer

(b) glitch

(c) master-slave flip-flop

(d) finite state machine

 
9. Write a single Verilog module to perform the following concurrent operations? (6 points)



## Computer Architecture ECE314 Winter 2004 Test 1

In each of the following problems, include comment lines at the start of each module with your name as author.

 10. Write a Verilog module for a 4-bit subtractor ( $F = A - B$ ). Simulate and verify the following cases: 9 - 3, 14 - 8, and 4 - 11. Paste your module code and a snapshot of the simulation waveform into one page of a Word document and attach a print-out to your exam. (15 points)
11. Write a structural Verilog module for the following logic operation. Use MAXPLUS to compile your module and submit a one-page screen shot showing the Verilog source and compilation window. (15 points)



12. Write a behavioral Verilog module for a JK flip-flop using an **always** statement. Use MAXPLUS to insure that your module compiles without errors. Submit a one-page screen shot showing the Verilog source and compilation window. (15 points)
13. Rewrite the following module to correct the syntax errors, and produce a successful compilation with MAXPLUS. Submit a one-page screen shot as before. (5 points)

```
module Exam-1(A,B,C,D,F)
inputs A, B, C;
Output D,F;
and g1(A,B,D);
not g2(D,B,A);
OR g3(F,B,C);
endmodule;
```