

# Computer Architecture ECE314

## Winter 2005 Test 1

1. The fundamental gates are NOT, AND, OR, XOR. Draw and label the corresponding logic symbols and Verilog operators? (8 points)
2. Identify the following terms or abbreviations (2 points each)
  - (a) ASCII
  - (b) BCD
  - (c) MSB
3. Convert  $38_{10}$  to octal, hexadecimal and binary. (6 points)
4. Convert the binary number 01001101 to an 8-bit 2's-complement negative number. (3 points)
5. What are the differences between a flip-flop and a latch? (2 points)
6. Explain the hierarchical nature of a computer system. (5 points)

7. Define or explain the following terms (3 points each)

(a) tri-state buffer

(b) gray code

(c) master-slave flip-flop

(d) finite state machine

8. How can you tell whether a Verilog module represents a state machine? (4 points)


9. Write a Verilog module to perform 2-1 multiplexor? (4 points)

## Computer Architecture ECE314

### Winter 2005 Test 1

In each of the following problems, include comment lines at the start of each module with your name as author.

 10. Write a structural Verilog module for the following logic operation. Use QUARTUS to compile your module and submit a one-page screen shot showing the Verilog source and compilation window. (20 points)



11. Write a behavioral Verilog module for a octal counter (0-7) using an **always** statement. Use QUARTUS to insure that your module compiles without errors. Submit a one-page screen shot showing the Verilog source and compilation window. (20 points)
12. Rewrite the following module to correct the syntax errors, and produce a successful compilation with QUARTUS. Submit a one-page screen shot as before. (10 points)

```
module 1st_exam(A,B,C,D,F)
inputs A, B, C;
Output D, F;
and g1(E,B,C);
not g2(d,E,A);
OR g1(F,B,C);
endmodule;
```